

## I List of Assignments:-

\* Refer to PART-A Sample Assignment.pdf for Order of contents in soft-copy.

Assignment Number	Assignment-Title	← Assignment Contents →									
		①	②	③	④	⑤	⑥	⑦	⑧	⑨	⑩
		BD	TT	MM	RTL-S	T-S	DUS	T-SUM	TBM	Sim	UCF
1	4-bit ALU	* Order of contents:- ① → ⑩ * All 10 compulsory for all 4									
2	4-bit USR										
3	FIFO/Memory										
4	FPGA - LCD I'face										

Contents:- ① → ⑩ abbreviations elaborated:-

- ① BD = Block Diagram
  - ② TT = Truth-Table / Function Table
  - ③ MM = Main (VHDL) Model
  - ④ RTL-S = RTL Schematic
  - ⑤ T-S = Technology Schematic
  - ⑥ DUS = Device Utilisation Summary
  - ⑦ T-SUM = Timing Summary
  - ⑧ TBM = TestBench (VHDL) Model
  - ⑨ Sim = Simulation w/f's
  - ⑩ UCF = User Constraint File
- } These are contained in Synthesis Report

\* Theory Section of PART-A Assignment


## II Assignment-wise BD's & TT's/FT's:-

Signal-names in BD are just for Illustration
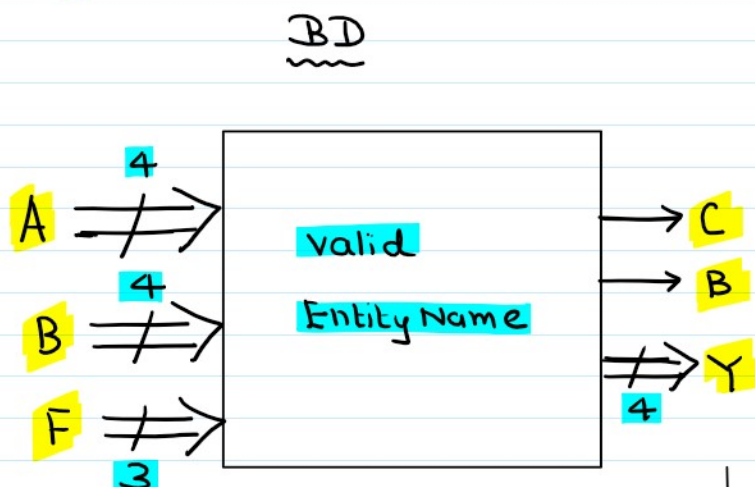
## II Assignment-wise BD's & TT's / FT's :-

★ Signal-names in BD are just for Illustration ★

① 4-bit ALU (Arithmetic Logic Unit) (2 Arithmetic, 6 logical operations)



- ★ A, B: 4-bit operands
- ★ F: 3-bit Function Bus (8 operations)
- ★ Y: 4-bit SUM/Difference/Logic O/p
- ★ C: Carry
- ★ B: Borrow

FT


Function Bus			Operations
F <sub>(2)</sub>	F <sub>(1)</sub>	F <sub>(0)</sub>	
0	0	0	• 2 Arithmetic Addition Subtraction
0	0	1	
0	1	0	• 6 Logical
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

★ There is Freedom of choice and order in 6 Logical operations

★ But all 8 operations cannot be Logical.

② 4-bit USR (Universal Shift Register) :-

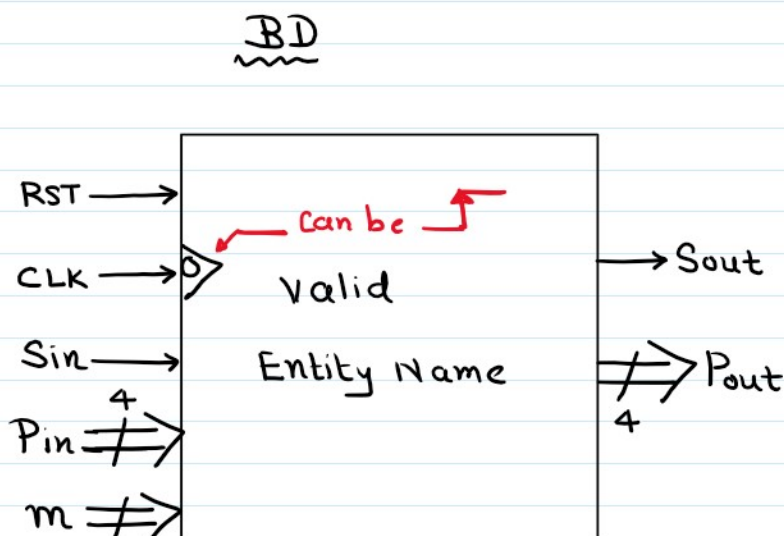(4 operations; Shifting can be RIGHT/LEFT)



FT

RST	CLK	m	Outputs/ mode
1	x	x	Sout = 0 Pout = 0000
0	↓	00	SISO
0	↓	01	SIPO
0	↓	10	PISO
0	↓	11	PIPO



\* Asynchronous Reset



\* Mode Latency (No. of clock cycles)

$$SISO = 4 + 4 = 8$$

$$SIPO = 4 + 1 = 5$$

$$PISO = 1 + 4 = 5$$

$$PIPO = 1 + 1 = 2$$

\* Power Hierarchy:-

Highest  
↓  
Lowest  
(Equal)

RST  
CLK  
MODE  
  
Sin, Pin



③ FIFO / 32-bit Memory (Organised as 4 x 8) :-

\* Can be a True FIFO (uses memory pointers, No address)

OR

\* Byte-Addressable Memory which can store 32-bits of data in form of 4 words, each 8-bit long (uses Address)

BD

  

FT


WRITE, READ are Active-High, Active-Low Resp.

rst	clk	wr_rd	d_out	full	empty
1	x	x	(00) <sub>16</sub>	0	1
0	↓	1	NA	0 → 1	0
0	↓	0	d-in	0	0

rst	clk	wr_rd	addr	d_out	full	empty
1	x	x	x	(00) <sub>16</sub>	0	1
0	↓	1	(00) <sub>2</sub>	NA	0 → 1	0
0	↓	0	↓	d-in	0	0



#### ④ LCD - FPGA Interfacing :-

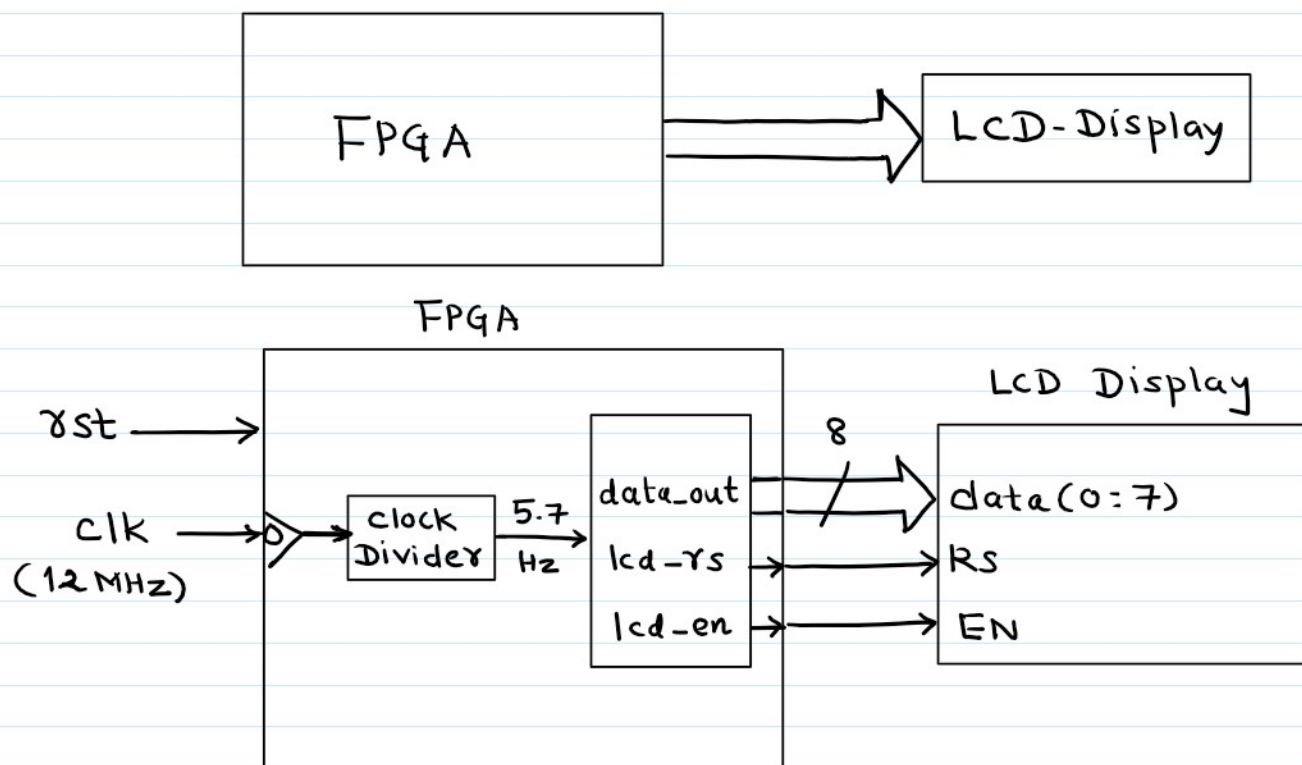

**Pin Assignment (UCF Location) for LCD:**

Signal Name	XC3S250E-PQ208	XCS6LX9-TQG144
LCD_RS	P48	P74
LCD_EN	P49	P72
LCD_Data0	P47	NC
LCD_Data1	P41	NC
LCD_Data2	P39	NC
LCD_Data3	P35	NC
LCD_Data4	P33	P66
LCD_Data5	P31	P61
LCD_Data6	P29	P59
LCD_Data7	P24	P58

Table 2.1: Pin Assignment (UCF) for LCD